

Laborbericht



Name	Sebastian Wenzel Grigorevski		
Praktikum	Hochfrequenzschaltungstechnik	Experiment Nr.	6
Matr. Nr.	35690104	Datum	10.2.2026


Für die Abgabe von Laborberichten im Fachgebiet Mikrowellenelektronik der Universität Kassel sind die Studierenden dazu verpflichtet die obenstehende Tabelle auszufüllen, die Eigenständigkeitserklärung zu lesen und mit Ihrer Unterschrift zu bestätigen. Die Titelseite muss mit einer einzelnen Heftklammer oben links an dem Bericht befestigt werden.
Bitte beantworten Sie jede Frage aus der Anleitung einzeln unter Angabe der entsprechenden Nummer aus der Anleitung.

Eigenständigkeitserklärung

Hiermit versichere ich, dass ich die folgende Arbeit selbstständig verfasst und keine anderen als die angegebenen Quellen und Hilfsmittel benutzt habe, alle Ausführungen, die anderen Schriften wörtlich oder sinngemäß entnommen wurden, kenntlich gemacht sind und die Arbeit in gleicher oder ähnlicher Fassung noch nicht Bestandteil einer Studien- oder Prüfungsleistung war. Hiermit bestätige ich, dass die nicht offengelegte Nutzung von auf generativer KI (Künstlicher Intelligenz) basierenden Hilfsmitteln als Plagiat gilt und zum Nichtbestehen führen kann.

Jeglicher im Bericht verwendeter, von KI erzeugter Text ist als direktes Zitat zu betrachten und muss daher durch Anführungszeichen und eine entsprechende Quellenangabe kenntlich gemacht werden. Die Quellenangabe muss Autor, Prompt, Herausgeber, Datum und die URL des verwendeten Tools enthalten. Ein Beispiel zur Zitierung von KI-generiertem Text finden Sie im Folgenden:

1. ChatGPT, Antwort auf "Erklär mir, wie man aus Haushaltszutaten einen Pizzateig zubereitet," OpenAI, März 7, 2023, <https://chat.openai.com/chat>.

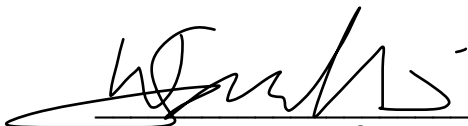
Datum, Unterschrift

Für weitere Informationen über Plagiate und zitation von KI, beachten Sie auch:

Plagiat und Täuschung: Information für Studierende

Universität Kassel, Abteilung Studium und Lehre | Prüfungsverwaltung, Status: 07/2023

Generative Artificial Intelligence: Citation and Attribution with AI Tools

Brown University Library, <https://libguides.brown.edu/AI>, Status: Okt. 14, 2025

Praktikum Hochfrequenz-Schaltungstechnik WS25/26

Bericht

Name:	Sebastian Grigorevski	Matrikelnr.:	35690104
Versuchsnr.:	6	Datum:	February 10, 2026

6.4.1

The load impedance $Z_L = 136\Omega - j34\Omega$ at $f = 145\text{ MHz}$ is matched to a system impedance of $Z_0 = 50\Omega$ using a series transmission line followed by a parallel transmission line.

First, the load impedance is normalized with respect to Z_0 and plotted in the Smith chart:

$$z_L = \frac{Z_L}{Z_0} = 2.72 - j0.68.$$

A series transmission line with characteristic impedance Z_0 is then added. Varying its length causes the reflection coefficient to rotate along a constant magnitude circle in the Smith chart. The length is chosen such that the transformed impedance intersects the admittance circle corresponding to 20 mS as can be seen in the figure below on the left. At this point, the impedance is converted to the admittance plane. A parallel transmission line is connected, and its length is adjusted to move the admittance along a constant admittance circle until the chart center is reached:

$$z = 1 + j0.$$

Thus the length of the series cable length is 24 cm and the parallel length is 31 cm to achieve this matching.

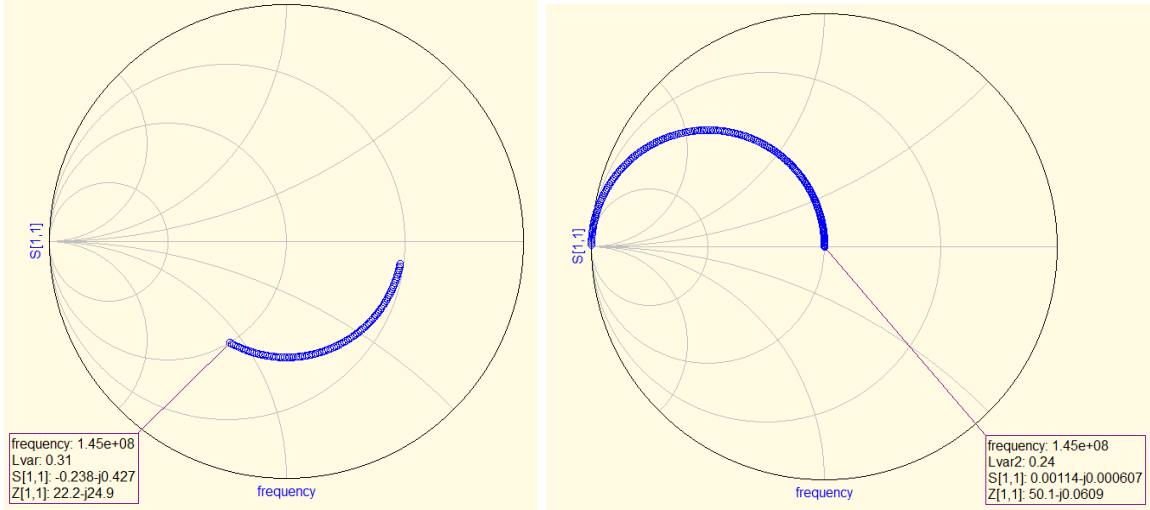


Figure 1: Reflection coefficient for increasing series cable length (left) and for increasing parallel cable length (right)

6.4.2

For the project *Parallelreihe*, the frequency range is determined in which the difference between the input impedance magnitude of the parallel RC network and its series equivalent remains below

$$|\Delta Z| < 0.2 \Omega$$

and simultaneously the phase difference satisfies

$$|\Delta \Phi| < 1^\circ.$$

From the figure 2 the frequency range that satisfies these conditions is determined at $f \in [0.95, 1.1]$ GHz for a 220Ω resistor. The figure shows the differences $\Delta Z = |Z_{\text{parallel}} - Z_{\text{series}}|$ and $\Delta \phi = |\phi_{\text{parallel}} - \phi_{\text{series}}|$ between the series and parallel circuits.

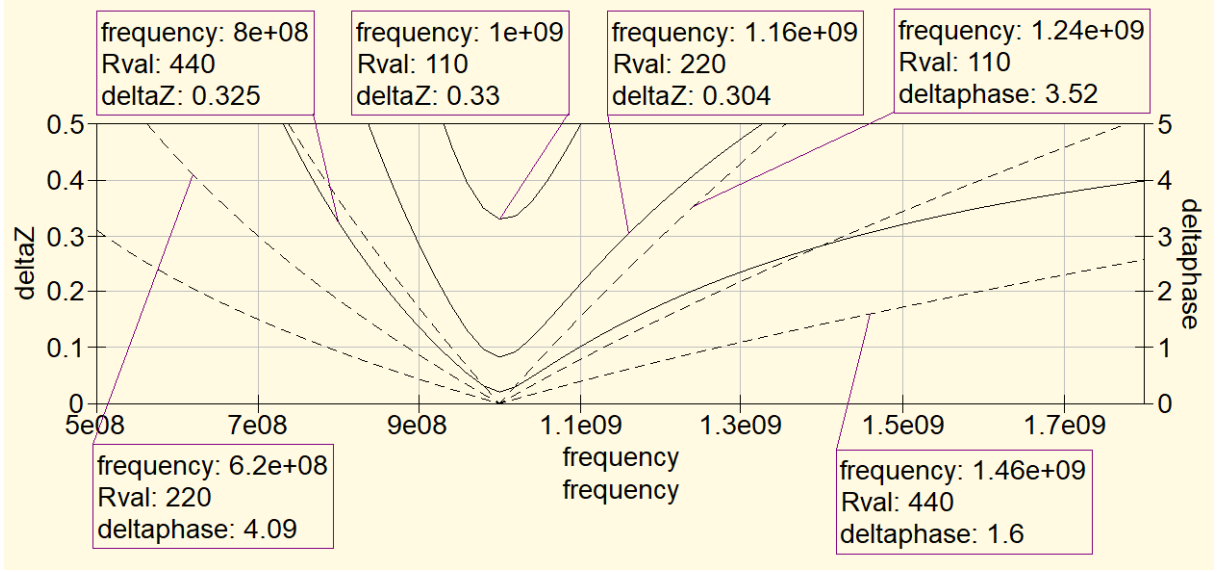


Figure 2: Difference in amplitude in Ω (solid) and phase in degree (dashed) between a parallel and series circuit as a function of frequency in Hz for different resistances R_{val}

When doubling or halving the quality factor by using 110 and 440 Ω as the parallel resistor and calculating its corresponding series circuits significant changes occur. Looking at the curves for 440 Ω or double the quality factor the frequency range is larger at $f \in [0.86, 1.24]$ GHz. On the other hand with 110 Ω the curve of the amplitude difference lays above the 0.2 Ω line while the phase curve is also narrower. This behavior supports the validity of the conversion formulas $R_{series} = R_{parallel}/Q^2$ and $X_{series} \approx X_{parallel}$ for quality factors $Q > 5$ since the frequency range decreases (diminishes) for smaller quality factors and increases for higher quality factors

6.4.3

For the matching network designed previously, the complex load impedance is removed and the reference port is shifted to the right side of the circuit. On the left side of the matching network, a resistor of $R = 50 \Omega$ is added to represent the internal resistance of the generator. At the design frequency of $f = 145$ MHz, the simulation yields an input impedance of

$$Z_{in} \approx 136 + j34 \Omega,$$

corresponding to a magnitude of approximately 140 Ω with a phase of 14.1°. The resulting input reflection coefficient is

$$|\Gamma| = X/R \approx 0.25,$$

indicating a partial mismatch.

This behavior arises because the matching network was designed to transform the complex load impedance into 50 Ω when viewed from the source side. Due to the reciproc

network, viewing it from the opposite direction results in the complex conjugate of the original load impedance rather than a matched condition.

The type of matching realized by this circuit is therefore a *conjugate impedance match*, which is valid only in the design direction and at a single frequency [1].

6.4.4

For a lossless transmission line, the input impedance is given by

$$Z_{\text{in}} = Z \frac{Z_L + jZ \tan(\beta l)}{Z + jZ_L \tan(\beta l)} [2].$$

At $l = \lambda/4$, $\tan(\beta l) \rightarrow \infty$, and the expression simplifies to

$$R_{\text{in}} = \frac{Z^2}{R_L} [2].$$

Simulations are performed for different real load resistances $R_L = 18 \Omega, 32 \Omega, 75 \Omega, 100 \Omega, 200 \Omega$ and different line impedances $Z = 30 \Omega, 40 \Omega, 50 \Omega, \sqrt{5000} \Omega, 100 \Omega$. In all cases, the simulated input resistance agrees with the analytical relation within small angle deviations as can be seen in table 1. At 300 MHz the wavelength is $\lambda = 1$ m, hence $\lambda/4 = 0.25$.

This result shows that a $\lambda/4$ transmission line inverts the load resistance. A low load resistance is transformed into a high input resistance and vice versa. By choosing

$$Z = \sqrt{R_S R_L},$$

a perfect impedance match between a source resistance R_S and the load can be achieved at the design frequency.

References

- [1] Dr. Schau. Resonanz und konjugierte komplexe anpassung. Technical report, Mitteilungen aus dem Institut für Umwelttechnik Nonnweiler-Saar, 2018. <http://do8ail.bplaced.net/db0fa/wordpress/wp-content/uploads/2018/05/Resonanz-und-konjugiert-komplexe-Anpassung.pdf> Accessed: 2026-01-29.
- [2] Wikipedia. Quarter-wave impedance transformer — Wikipedia, the free encyclopedia. <http://en.wikipedia.org/w/index.php?title=Quarter-wave%20impedance%20transformer&oldid=1250525105>, 2026. [Online; accessed 30-January-2026].

Table 1: Simulated and analytical input resistance of a $\lambda/4$ transformer at $f = 300$ MHz

$Z_{\text{line}} [\Omega]$	$R_L [\Omega]$	$f [\text{Hz}]$	$Z_{11} (\text{sim.}) [\Omega/^\circ]$	$R_{\text{in,th}} [\Omega]$
30	18	3×10^8	50/ -0.0665°	50
30	32	3×10^8	28.1/ 0.00805°	28.1
30	75	3×10^8	12/ 0.131°	12
30	100	3×10^8	9/ 0.189°	9
30	200	3×10^8	4.5/ 0.406°	4.5
40	18	3×10^8	88.9/ -0.11°	88.9
40	32	3×10^8	50/ -0.028°	50
40	75	3×10^8	21.3/ 0.0836°	21.3
40	100	3×10^8	16/ 0.131°	16
40	200	3×10^8	8/ 0.299°	8
50	18	3×10^8	139/ -0.151°	138.9
50	32	3×10^8	78.1/ -0.0575°	78.1
50	75	3×10^8	33.3/ 0.0519°	33.3
50	100	3×10^8	25/ 0.0935°	25
50	200	3×10^8	12.5/ 0.234°	12.5
70.7	18	3×10^8	278/ -0.229°	277.8
70.7	32	3×10^8	156/ -0.109°	156.3
70.7	75	3×10^8	66.7/ 0.00734°	66.7
70.7	50	3×10^8	100/ -0.0441°	100
70.7	100	3×10^8	50/ 0.0441°	50
70.7	200	3×10^8	25/ 0.154°	25
100	18	3×10^8	556/ -0.335°	555.6
100	32	3×10^8	312/ -0.175°	312.5
100	75	3×10^8	133/ -0.0363°	133.3
100	50	3×10^8	200/ -0.0935°	200
100	100	3×10^8	100/ $1.4 \times 10^{-17^\circ}$	100
100	200	3×10^8	50/ 0.0935°	50